

A decorative graphic on the left side of the slide, consisting of a network of white lines and circles on a blue gradient background. The lines are vertical and horizontal, with some diagonal segments, and the circles are of varying sizes, resembling a circuit board or a digital network.

DIGITAL DESIGN

LAB12 FREQUENCY DIVIDER AND ITS APPLICATION (PROJECT RELATED)

WANGW6@SUSTECH.EDU.CN

LAB12

- Frequency Divider
 - Divide by even
 - Divide by odd
- Structure Design and Frequency Divider
 - Flowing light
 - 7-seg tube

WANGW6@SUSTECH.EDU.CN

CLOCK ON EGO1/MINISYS BOARD

The **100Mhz** is the most common basic clock frequency. We usually perform frequency division processing based on this frequency to obtain the clock we need.

- **EGO1** board includes a **100MHz** crystal oscillator connected to the main chip **P17** pin.
- **Minisys** board includes a **100MHz** crystal oscillator connected to the main chip **Y18** pin.

FREQUENCY DIVIDER

- A **Frequency Divider**, also called a **clock divider** or scaler or pre-scaler, is a circuit that takes an input signal of a frequency f_{in} , and generates an output signal of a frequency f_{out} :

$$f_{out} = f_{in}/n \text{ (n is an integer).}$$

- For power-of-2 integer division, a simple binary counter can be used, clocked by the input signal. The least-significant output bit alternates at 1/2 the rate of the input clock, the next bit at 1/4 the rate, the third bit at 1/8 the rate, etc.
- An arrangement of flipflops is a classic method for integer-n division. Such division is frequency and phase coherent to the source over environmental variations including temperature. The easiest configuration is a series where each flip-flop is a divide-by-2. For a series of three of these, such system would be a divide-by-8. By adding additional logic gates to the chain of flip flops, other division ratios can be obtained. Integrated circuit logic families can provide a single chip solution for some common division ratios.


FREQUENCY DIVIDER(N:4)

```
`timescale 1ns / 1ps

module clk_div(input clk,rst_n,output reg clk_out);
    parameter period = 4;
    reg [3:0] cnt;
    always@(posedge clk,negedge rst_n)
    begin
        if(~rst_n)begin
            cnt <=0;
            clk_out<=0;
        end
        else
            if(cnt==((period>>1) - 1)) begin
                clk_out <= ~clk_out;
                cnt <=0;
            end
            else begin
                cnt <= cnt+1;
            end
        end
    end
endmodule
```

```
`timescale 1ns / 1ps

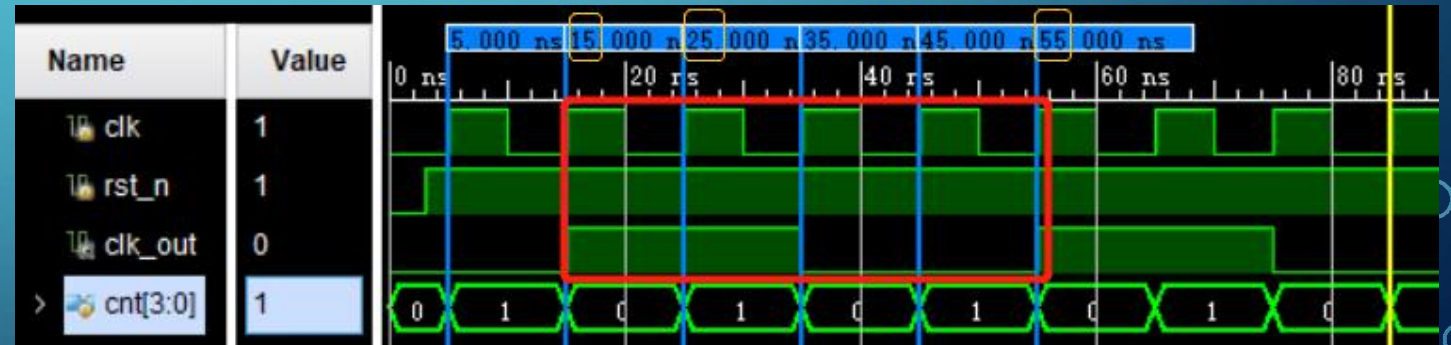module clk_div_tb( );
    reg clk,rst_n;
    wire clk_out;
    clk_div cd(clk,rst_n,clk_out);
    initial fork
        clk <=0;
        rst_n <=0;
        # 3 rst_n <= 1;
        forever
            #5 clk = ~clk;
    join
endmodule
```



FREQUENCY DIVIDER(N:5)

```

timescale 1ns / 1ps
module clock_div(input clk,rst_n,output reg clk_out );
//reg [25:0]cnt;...
reg [2:0] step1,step2;
always@(posedge clk)begin
    if(~rst_n)begin
        step1<=3'b000;
    end
    else begin
        case(step1)
            3'b000: step1<=3'b001;
            3'b001: step1<=3'b011;
            3'b011: step1<=3'b100;
            3'b100: step1<=3'b010;
            3'b010: step1<=3'b000;
            default:step1<=3'b000;
        endcase
    end
end
end

```

```
assign clk_out=step1[0]|step2[0];
```

```

always @(negedge clk,negedge rst_n)
    if(~rst_n)
        step2<=3'b000;
    else
        case(step2)
            3'b000: step2<=3'b001;
            3'b001: step2<=3'b011;
            3'b011: step2<=3'b100;
            3'b100: step2<=3'b010;
            3'b010: step2<=3'b000;
            default:step2<=3'b000;
        endcase
    end
endmodule


```

```

timescale 1ns / 1ps
////////////////////////////////////

module clock_div_tb( );
reg clk,rst_n;
wire clk_out;
clock_div cd(clk,rst_n,clk_out);
initial fork
    clk <=0;
    rst_n <=0;
    # 3 rst_n <= 1;
    forever
        #5 clk = ~clk;
join
endmodule


```

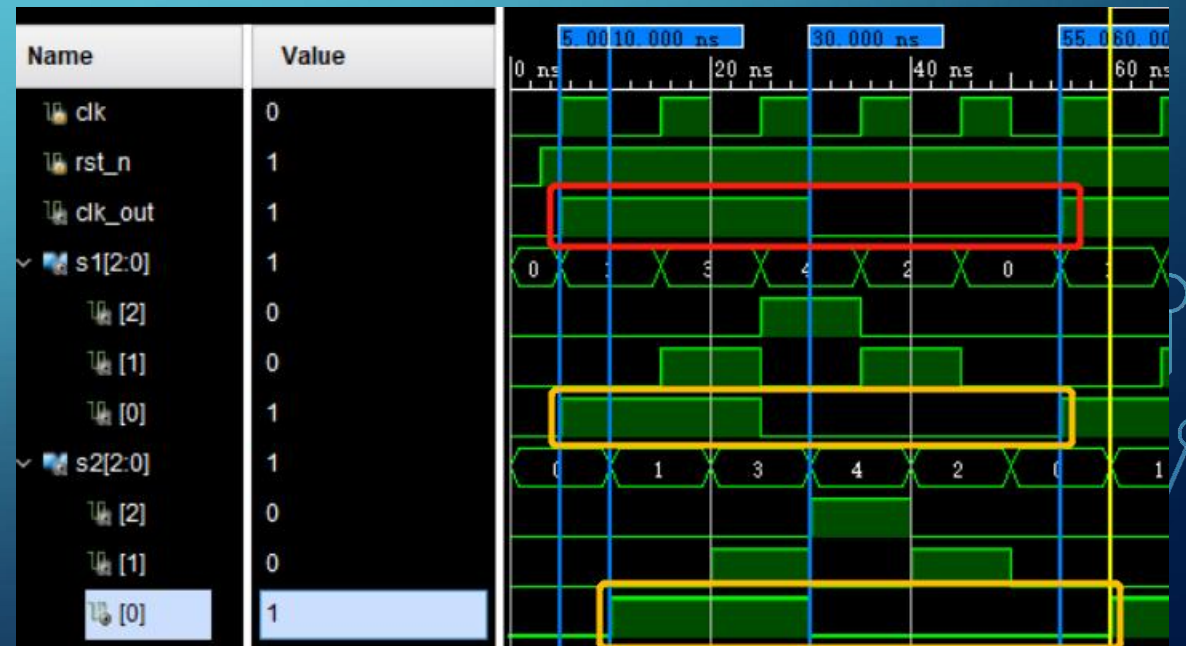

DEMO1:FLOWING LIGHT1(1)

```
`timescale 1ns / 1ps
module flowing_light_lite(input clk,rst_n,output[7:0] led);
    reg [7:0] light_reg;
    always@(posedge clk,negedge rst_n)
    begin
        if(!rst_n)
            light_reg<=8'b0000_0001;
        else if(light_reg == 8'b1000_0000)
            light_reg<=8'b0000_0001;
        else
            light_reg<=light_reg<<1;
    end
    assign led = light_reg;
endmodule
```

```
`timescale 1ns / 1ps
module flow_water_tb( );
    reg clk,rst_n;
    wire [7:0]led;
    //flow_water_lights fs(clk,rst_n,led,cnt,ns);
    flowing_light_lite fs(clk,rst_n,led);
    initial fork
        rst_n <=1'b0;
        clk <= 1'b0;
        #2 rst_n <=1'b1;
        forever
            #5 clk = ~clk;
    join
endmodule
```

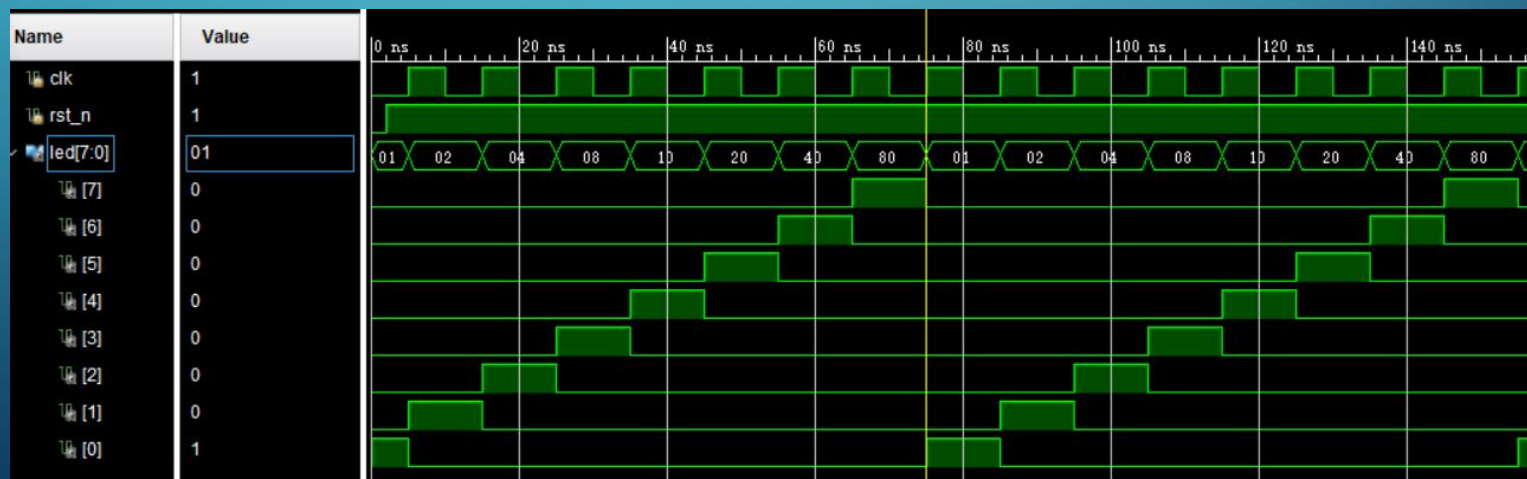

DEMO1:FLOWING LIGHT1(2)

```
`timescale 1ns / 1ps
module flowing_light_lite(input clk,rst_n,output[7:0] led);
    reg [7:0] light_reg;
    always@(posedge clk,negedge rst_n)
    begin
        if(!rst_n)
            light_reg<=8'b0000_0001;
        else if(light_reg == 8'b1000_0000)
            light_reg<=8'b0000_0001;
        else
            light_reg<=light_reg<<1;
    end
    assign led = light_reg;
endmodule
```

Before creat the constraints file with the circuit, generate the bitstream file and program it on the FPGA chip of the board, think about the following question:

1. “**rst_n**” is high effective or low effective?
Is it a synchronous reset signal or an asynchronous reset signal?
Which is more suitable for the “rst_n”, a **switch** or a **button** ?
2. If the “**clk**” is binded with pin “p17” of EGO1, How long does a cycle last based on the “clk”?
could it be recognized by human eyes?
3. While replace the operator “<<” with “<<<” in the code on the left hand, will the updated circuit work same as the original one?

DEMO2: FLOWING LIGHT2(1)

The clock frequency of 100Mhz is too fast to be recognized by human eyes. The 100Mhz clock need frequency division.

```
timescale 1ns / 1ps
module flash_led_top(
    input clk,
    input rst_n,
    input sw0,
    output [7:0] led
);

    wire clk_bps;
    counter counter(
        .clk( clk ),
        .rst_n( rst_n ),
        .clk_bps( clk_bps )
    );
    flash_led_ctl flash_led_ctl(
        .clk( clk ),
        .rst_n( rst_n ),
        .dir( sw0 ),
        .clk_bps( clk_bps ),
        .led( led )
    );
endmodule
```

```
21 module counter(
22     input clk,
23     input rst_n,
24     output clk_bps
25 );
26     reg [13:0] cnt_first, cnt_second;
27     always@(posedge clk, negedge rst_n)
28         if( !rst_n )
29             cnt_first <= 14'd0;
30         else if (cnt_first == 14'd10000)
31             cnt_first <= 14'd0;
32         else
33             cnt_first <= cnt_first + 1'b1;
34     always@(posedge clk, negedge rst_n)
35         if( !rst_n )
36             cnt_second <= 14'd0;
37         else if (cnt_second == 14'd10000)
38             cnt_second <= 14'd0;
39         else if ( cnt_first == 14'd10000)
40             cnt_second <= cnt_second + 1'b1;
41         else
42             cnt_second <= cnt_second;
43     assign clk_bps = cnt_second == 14'd10000;
44 endmodule
```

```
21 module flash_led_ctrl(
22     input clk,
23     input rst_n,
24     input dir,
25     input clk_bps,
26     output reg[7:0] led
27 );
28     always@(posedge clk or negedge rst_n)
29         if( !rst_n )
30             led <= 8'h80;
31         else
32             case( dir )
33                 1'b0:
34                     if(clk_bps)
35                         if( led != 8'h01 )
36                             led <= led >> 1'b1; //shift right
37                     else
38                         led <= 8'h80;
39                 1'b1:
40                     if(clk_bps)
41                         if( led != 8'h80 )
42                             led <= led << 1'b1; //shift left
43                     else
44                         led <= 8'h01;
45             endcase
46 endmodule
```

DEMO2: FLOWING LIGHT2(2)



NOTES:

1. While test the circuit by simulation, the default simulation time(1000ns) need to be longer.
2. While test the circuit by the board, Different constraint files are required according to the type of board(EGO1 or Minisys).


The pin of clock(100MHZ) on EGO1 board

```
set_property PACKAGE_PIN P17 [get_ports clk]
```

The pin of clock(100MHZ) on Minisys board

```
set_property PACKAGE_PIN Y18 [get_ports clk]
```


DEMO3 : 7-SEG TUBE(1)

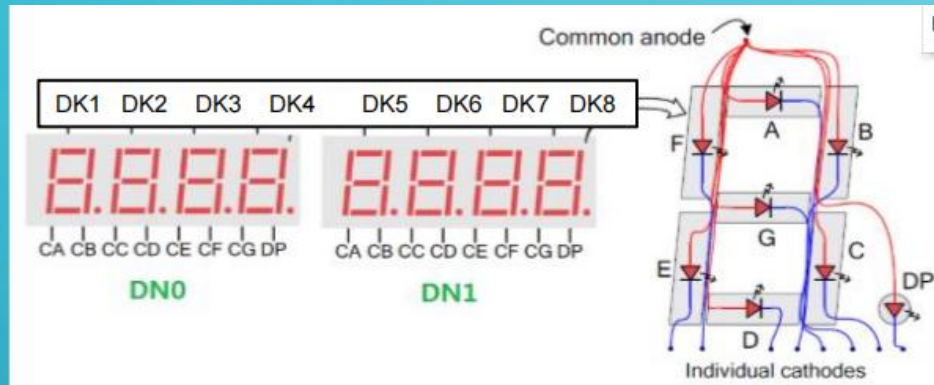

7-seg Tube: There are 2 group 7seg tubes on EGO1, each group share the same controller bits.


TASK:

Display 8 different numbers on 8 7seg tubes of EGO1 board.

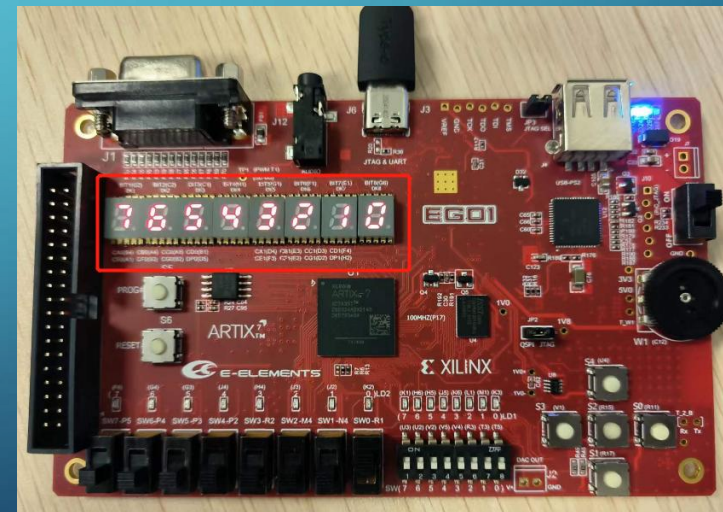


DEMO3 : 7-SEG TUBE(2)

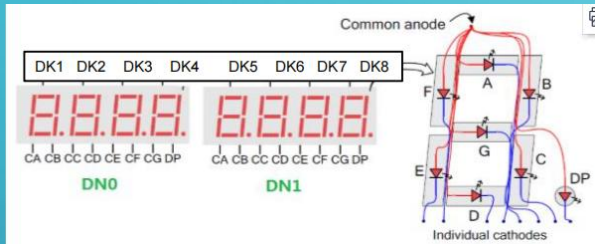The code on the right hand is from lab8, the circuit reads the data from switch and show the number on the 7seg tubes .



```
module light_7seg_ego1(input [3:0]sw,output reg [7:0] seg_out, output [7:0] seg_en);
    assign seg_en = 8'hff;
    always @ *
        case(sw)
            4'h0: seg_out = 8'b1111_1100; //0
            4'h1: seg_out = 8'b0110_0000; //1
            4'h2: seg_out = 8'b1101_1010; //2
            4'h3: seg_out = 8'b1111_0010; //3
            4'h4: seg_out = 8'b0110_0110; //4
            4'h5: seg_out = 8'b1011_0110; //5
            4'h6: seg_out = 8'b1011_1110; //6
            4'h7: seg_out = 8'b1110_0000; //7
            4'h8: seg_out = 8'b1111_1110; //8
            4'h9: seg_out = 8'b1110_0110; //9
            4'ha: seg_out = 8'b1110_1110; //A
            4'hb: seg_out = 8'b0011_1110; //B
            4'hc: seg_out = 8'b1001_1100; //C
            4'hd: seg_out = 8'b0111_1010; //D
            4'he: seg_out = 8'b1001_1110; //E
            4'hf: seg_out = 8'b1000_1110; //F
            default: seg_out = 8'b0000_0001;
        endcase
    endmodule
```


DEMO2 : 7-SEG TUBE(3)

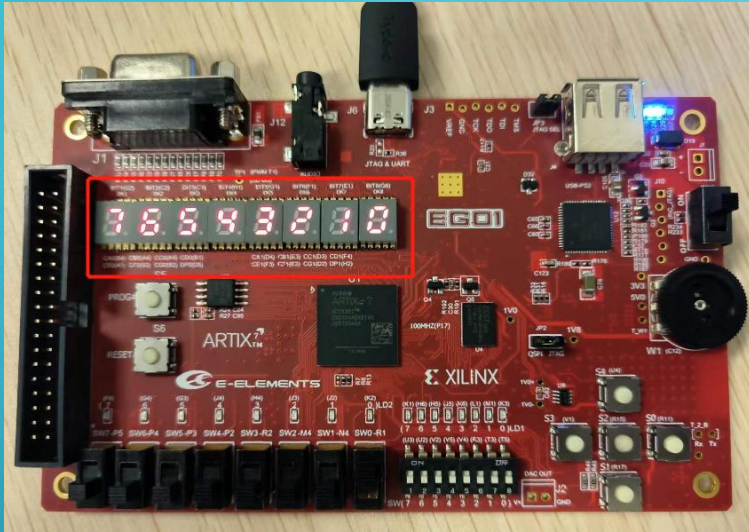

Display different numbers on 8 7seg tubes of EGO1 board.

Tips:

1. There are 2 group 7seg tubes on EGO1, each group share the same cttroller bits.
2. The code of lab8 could be used in this exercise.

WANGW6@SUSTECH.EDU.CN

```
module scan_seg( rst_n, clk, seg_en, seg_out0, seg_out1 );
    input rst_n ; //reset: low effective
    input clk ; //system clock 100MHZ
    output reg [7:0] seg_en ; // selection on tube 0-7
    output [7:0] seg_out0; // seg0 selection
    output [7:0] seg_out1; // seg1 selection

    reg clkout;
    reg [31:0] cnt;
    reg [2:0] scan_cnt;

    parameter period = 200000; //500HZ stable
    // parameter period = 250000; //400HZ stable
    // parameter period = 5000000; //20HZ loop one by one
    // parameter period = 2500000; //40HZ twinkle
    // parameter period = 1000000; //100HZ twinkle

    always @(posedge clk, negedge rst_n) //frequency division : clk -> clk_out...
    always @(posedge clkout, negedge rst_n) //change scan_cnt based on clkout...
    always @ ( scan_cnt) //select tube...

    //module light_7seg_ego1(input [3:0]sw, output reg [7:0] seg_out, output [7:0] seg_en);
    wire [7:0] useless_seg_en0, useless_seg_en1;
    light_7seg_ego1 u0(.sw({1'b0, scan_cnt}), .seg_out(seg_out0), .seg_en(useless_seg_en0));
    light_7seg_ego1 u1(.sw({1'b0, scan_cnt}), .seg_out(seg_out1), .seg_en(useless_seg_en1));
endmodule
```

DEMO3 : 7-SEG TUBE(4)

In this situation, should the clock frequency be as fast as possible, or as slow as possible ?

```
parameter period = 200000; //500HZ stable
// parameter period = 250000; //400HZ stable
// parameter period = 5000000; //20HZ loop one by one
// parameter period = 2500000; //40HZ twinkle
// parameter period = 1000000; //100HZ twinkle

always @(posedge clk, negedge rst_n) //frequency division : clk -> clk_out
begin
    if(!rst_n) begin
        cnt <= 0;
        clkout <= 0;
    end
    else begin
        if (cnt == (period>>1)-1)
            begin
                clkout <= ~clkout;
                cnt <= 0;
            end
        else
            cnt <= cnt+1;
        end
    end
end
```


```
always @(posedge clkout, negedge rst_n) //change scan_cnt based on clkout
begin
    if(~rst_n)
        scan_cnt <= 0;
    else begin
        if(scan_cnt==3'd7)
            scan_cnt <= 0;
        else
            scan_cnt <= scan_cnt + 1;
        end
    end
end
always @ ( scan_cnt) //select tube
begin
    case (scan_cnt)
        3'b000 : seg_en = 8'h01;
        3'b001 : seg_en = 8'h02;
        3'b010 : seg_en = 8'h04;
        3'b011 : seg_en = 8'h08;
        3'b100 : seg_en = 8'h10;
        3'b101 : seg_en = 8'h20;
        3'b110 : seg_en = 8'h40;
        3'b111 : seg_en = 8'h80;
        default: seg_en = 8'h00;
    endcase
end
```

PRACTICE1,2

- 1. Implement a 'Breathing lamp' on EGO1 board, the 'Breathing lamp' here is a led which light on for 1 seconds while light off for 1 seconds.
- 2. The starting switch of the induction cooker is equipped with a child lock button. The button will not take effect until it is pressed continuously for 2 second. Within 1 second of the child lock button taking effect, the induction cooker can be started only after the start switch is turned on, otherwise the induction cooker cannot be started. Implement the circuit to turn on the induction cooker.

PRACTICE3

 - 3-1 Show the detailed information about the input and output devices used in the EGO1 development board for the project(refer to the image on the right for reference)
- 3-2 show the team's development plan (work in each stage)



TIPS

If you have any problem about frequency divider, wish this demo will help you.
2-stages is an easier way for understanding sequential circuit compared to 1-stage.

```
module clk_div_2(input clk,rst_n,output reg clk_out );

    parameter period=4;
    reg [3:0] cnt;
    reg [3:0] cnt_ns;
    reg clk_out_ns;
    always@(posedge clk,negedge rst_n)...

    always@(*)begin...

    always@(posedge clk,negedge rst_n)...

    always@(*)...
endmodule
```

```
always@(posedge clk,negedge rst_n)
begin
    if(~rst_n)begin...
    else
        clk_out<=clk_out_ns;
    end

    always@(*)begin
    if(~rst_n)
        clk_out_ns = 1;
    else
        if(cnt==((period>>1)-1))
            clk_out_ns = ~clk_out;
        else
            clk_out_ns = clk_out;
        end
    end
```

```
always@(posedge clk,negedge rst_n)
begin
    if(~rst_n)begin
        cnt<=0;
    end
    else begin
        cnt<=cnt_ns;
    end
end

always@(*)
begin
    if(cnt==((period>>1)-1))
        cnt_ns=0;
    else
        cnt_ns=cnt+1;
    end
```

